

CMP-3002A
Foundations of Computing 1

Week 9:

Circuits & Controllers

Dr Robert Blair

r.blair@uea.ac.uk

Introduction to basic analogue electronics


Outline

1. Recap: Basic circuits
2. Micro Controller
3. Building circuits
4. Schematic circuit diagrams
5. 'Pull Down' resistor
6. 'Pull Up' resistor
7. State comparison
8. Input Comparison
9. Examples


Learning outcomes

- You will be able to define a basic circuit
- You will be able to explain the concept of a programmable controller
- You will be able to define Pull-Up and Pull-Down resistors and their use
- You will be able to write code to create 'Toggle' switch effect
- You will be able to write code which uses input comparison

Basic Circuits

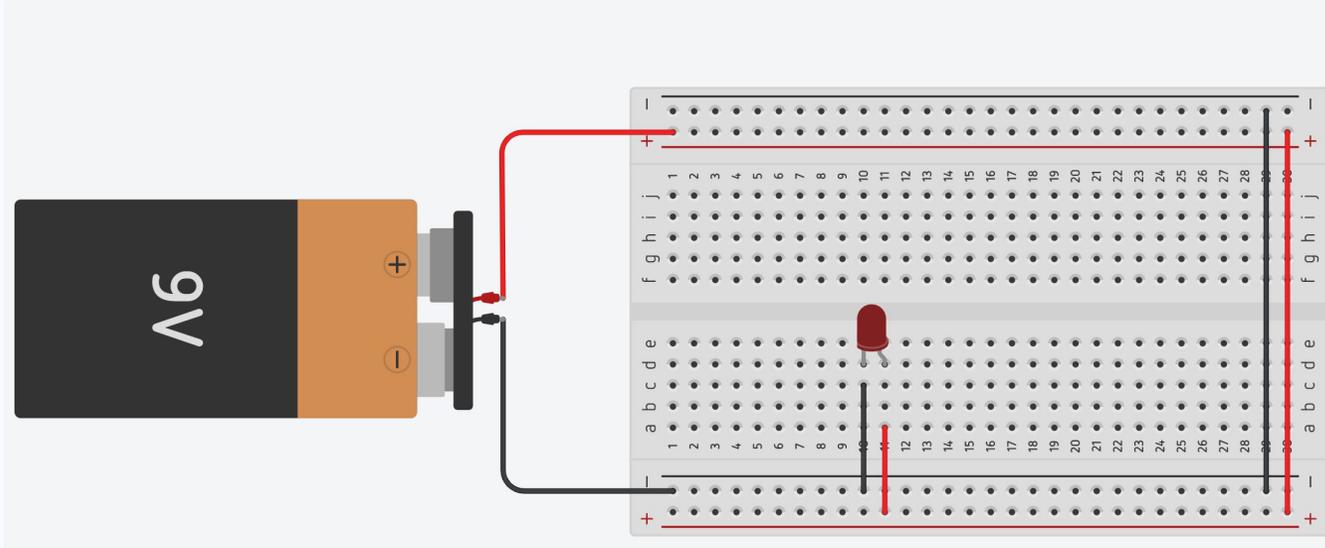


Circuit view

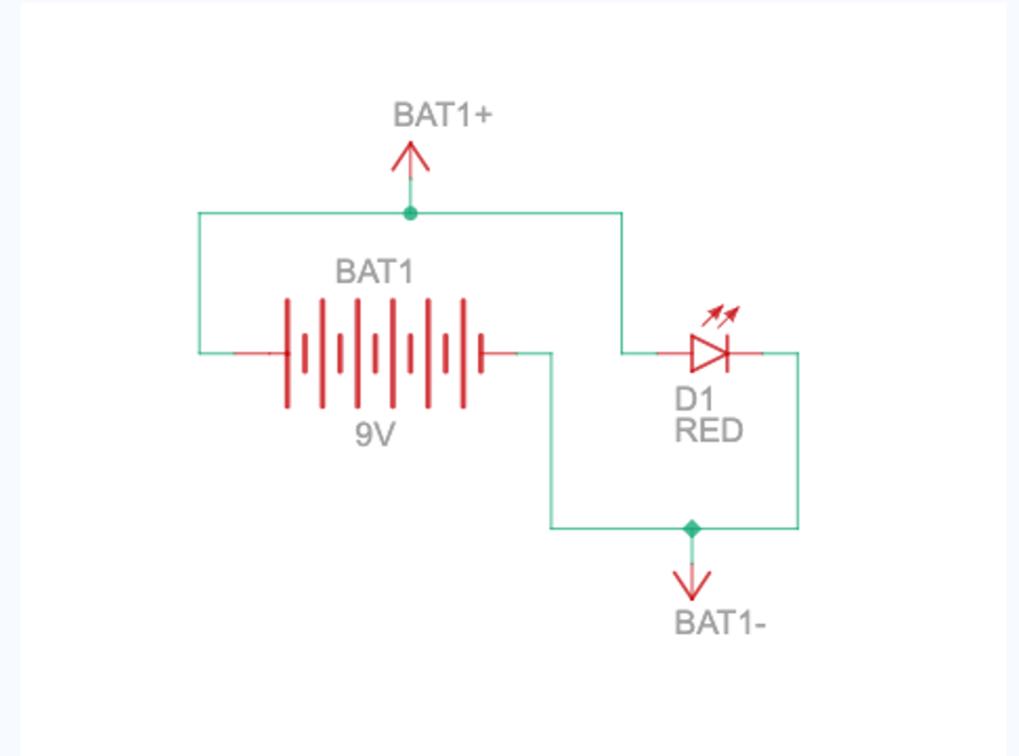

Schematic view

Power source, connectors, breadboard, LED


Basic Circuits – oops!

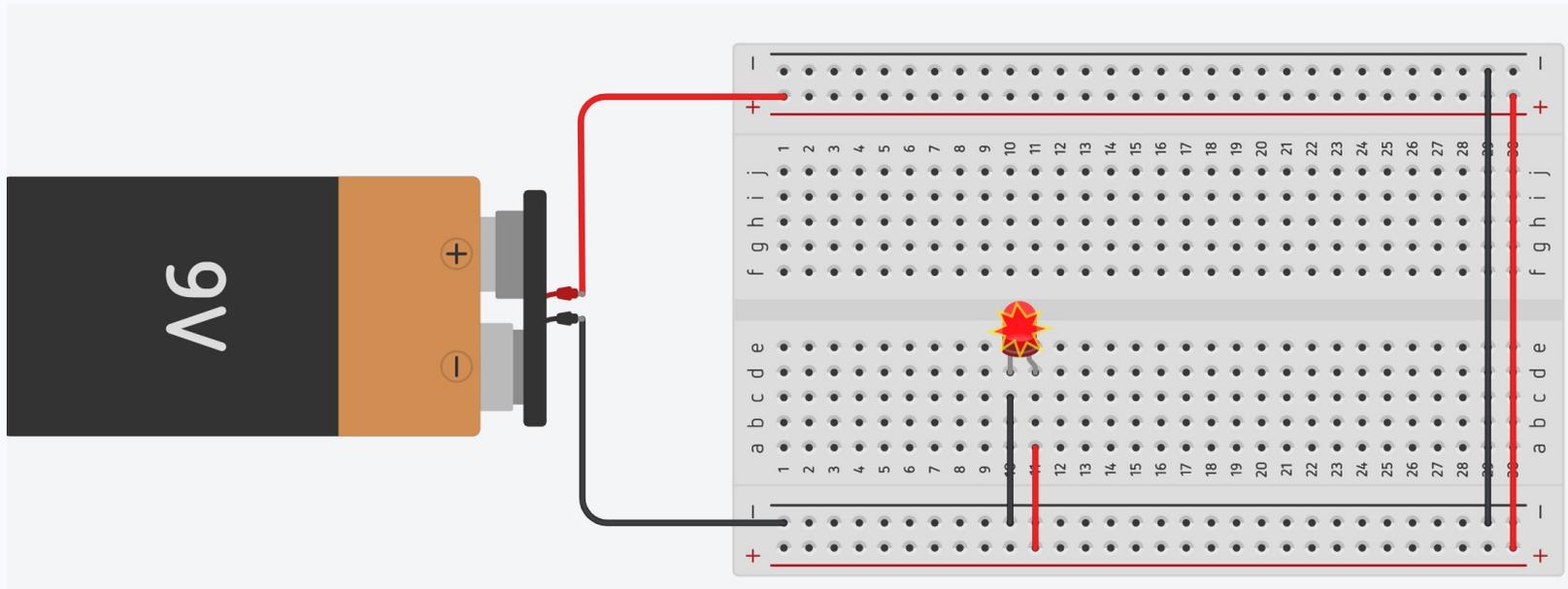

Circuit view

Power source, connectors, breadboard, LED


Basic Circuits – that's better.

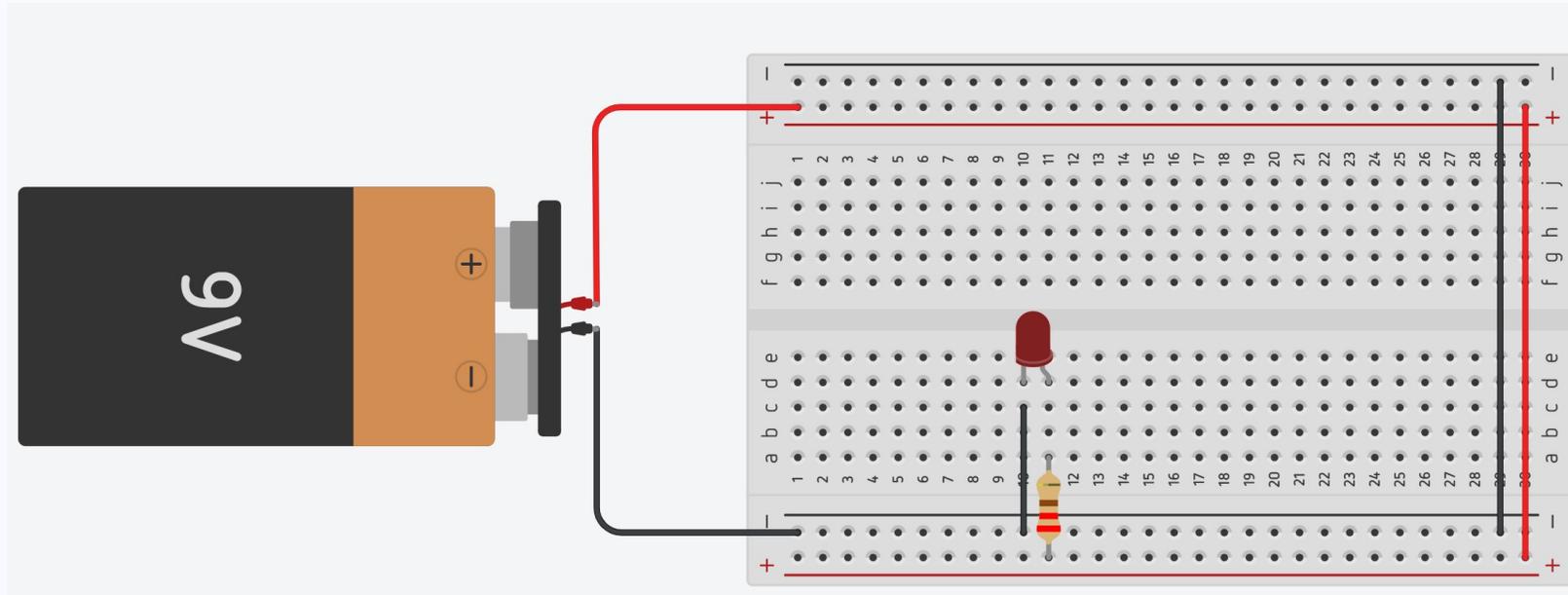


Circuit view

Power source, connectors, breadboard, LED, resistor

Basic Circuits – control

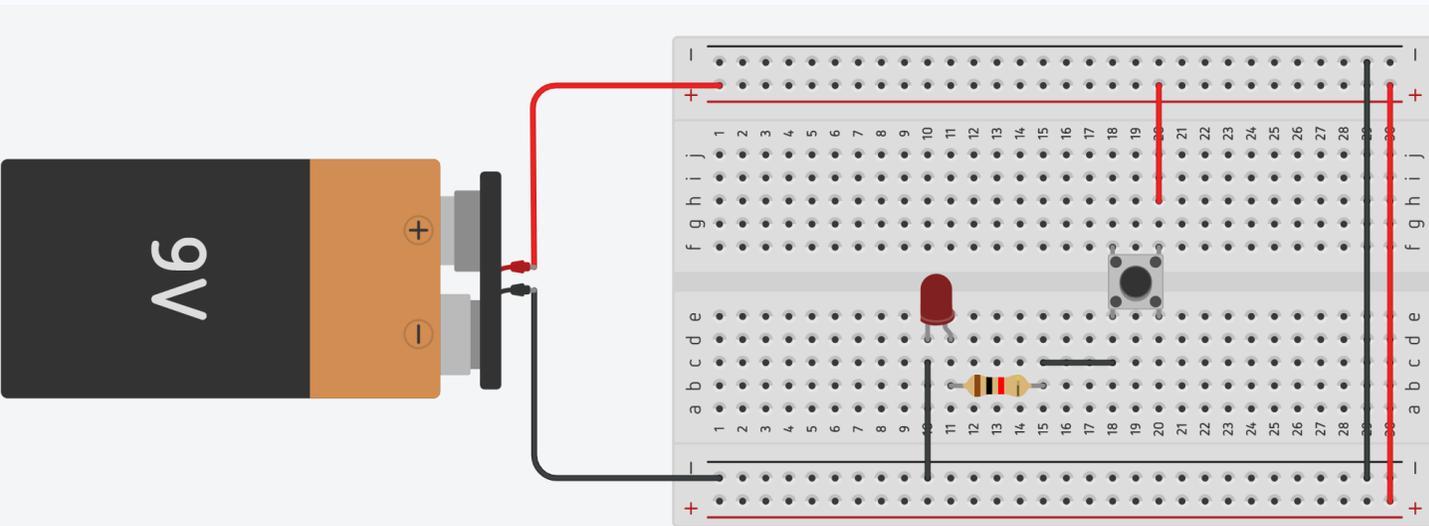


Circuit view

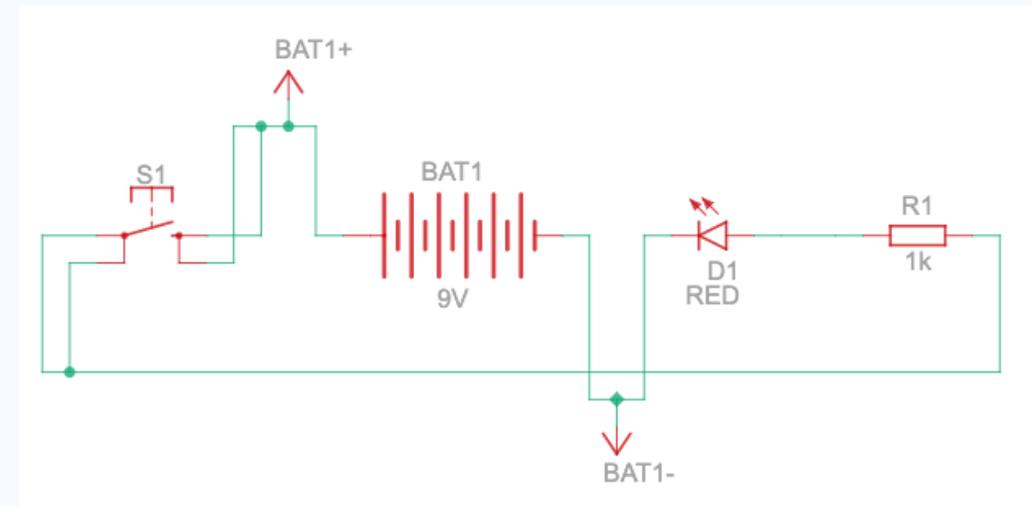

Schematic view

Power source, connectors, breadboard, LED

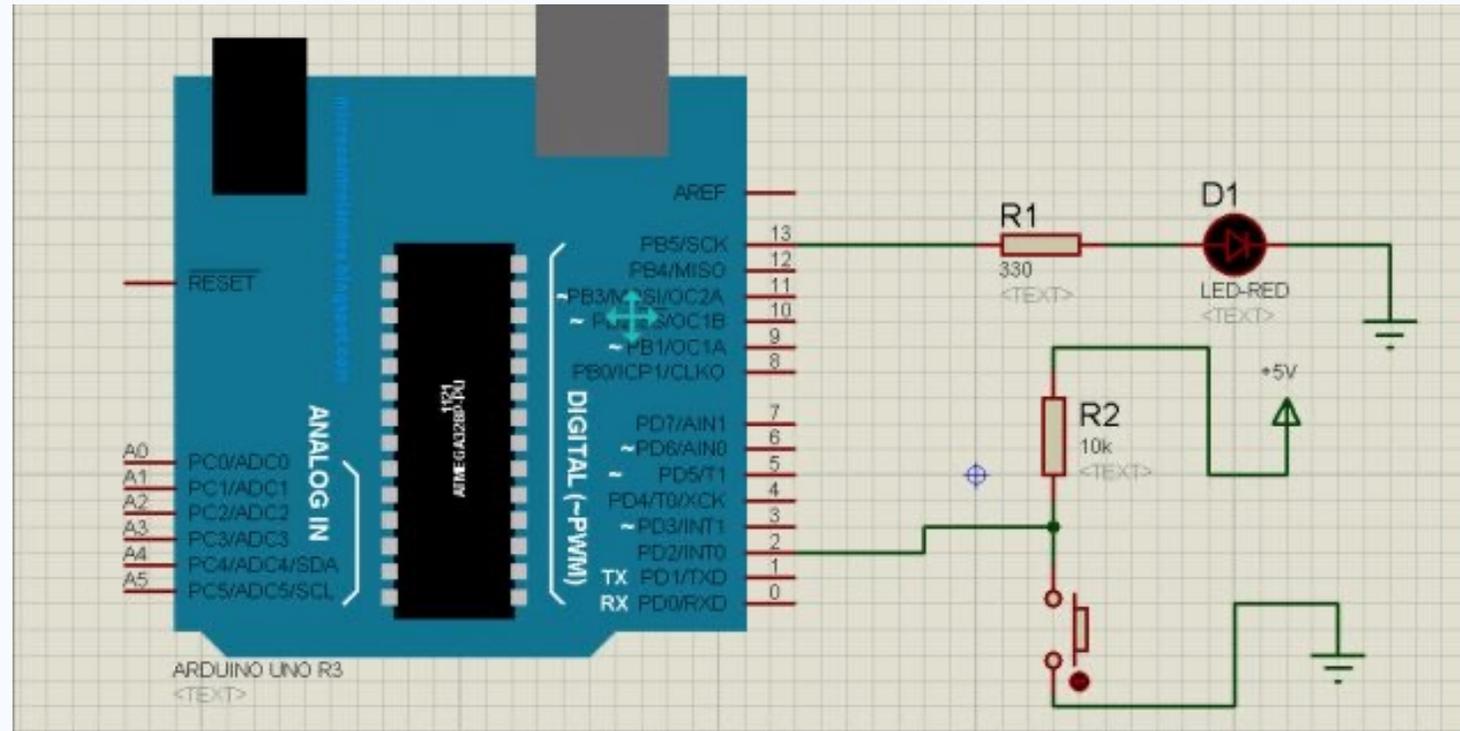Basic Circuits – Switch (pull up resistor)




<https://www.electronicclinic.com/arduino-push-button-switch-wiring-and-code-beginners-level/>

Schematic view – `'pinMode(PUSH_BUTTON,INPUT_PULLUP);'`

The PULLUP resistor configuration is the opposite of the PULLDOWN resistor configuration. In normal condition 5 volts are connected with the Arduino's pin and when the Push Button is press then ground is connected with the Arduino's pin.

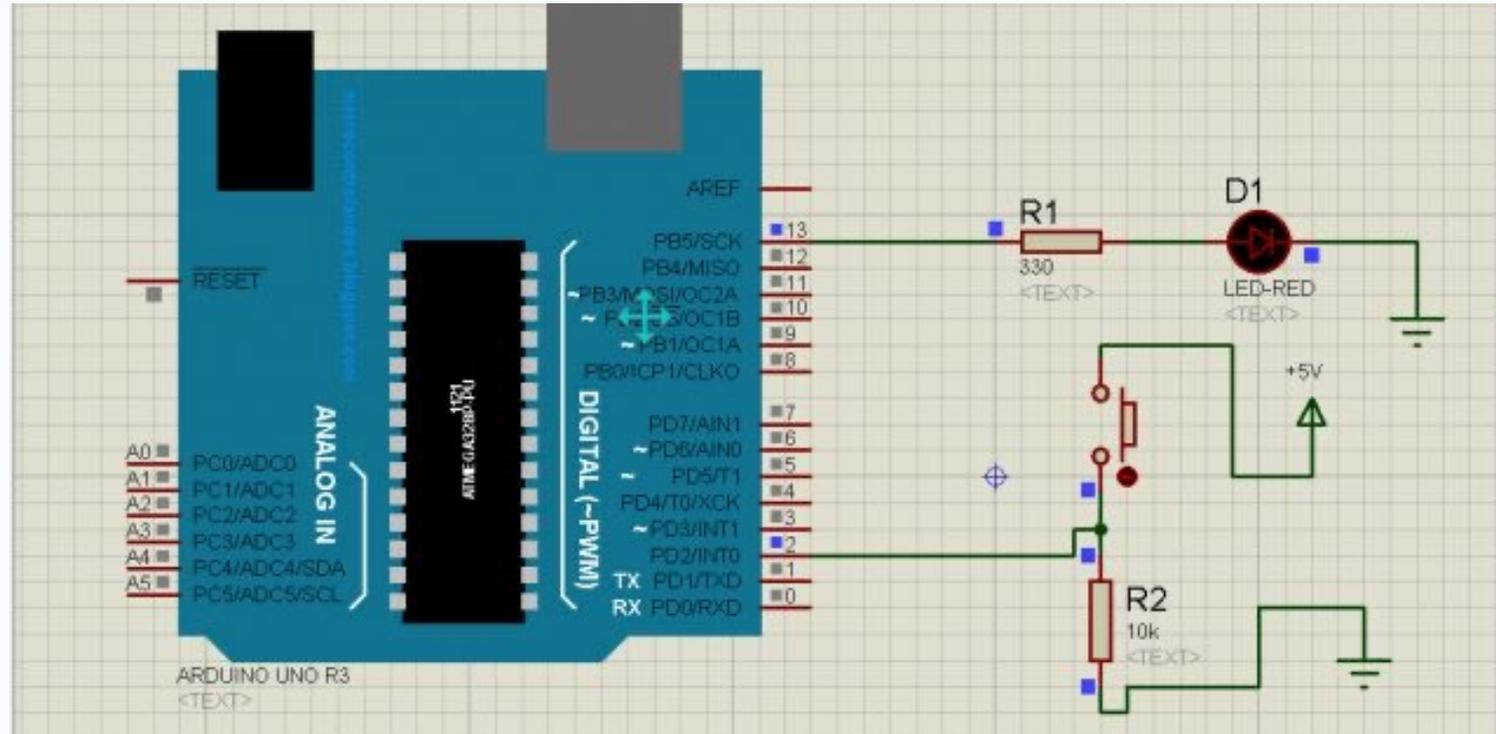Basic Circuits – Switch (pull down resistor)




<https://www.electronicclinic.com/arduino-push-button-switch-wiring-and-code-beginners-level/>


Schematic view

When you press the button it gives 5 volts to the Arduino pin and when you release the button it gives ground to the Arduino's pin.

Basic Circuits – components

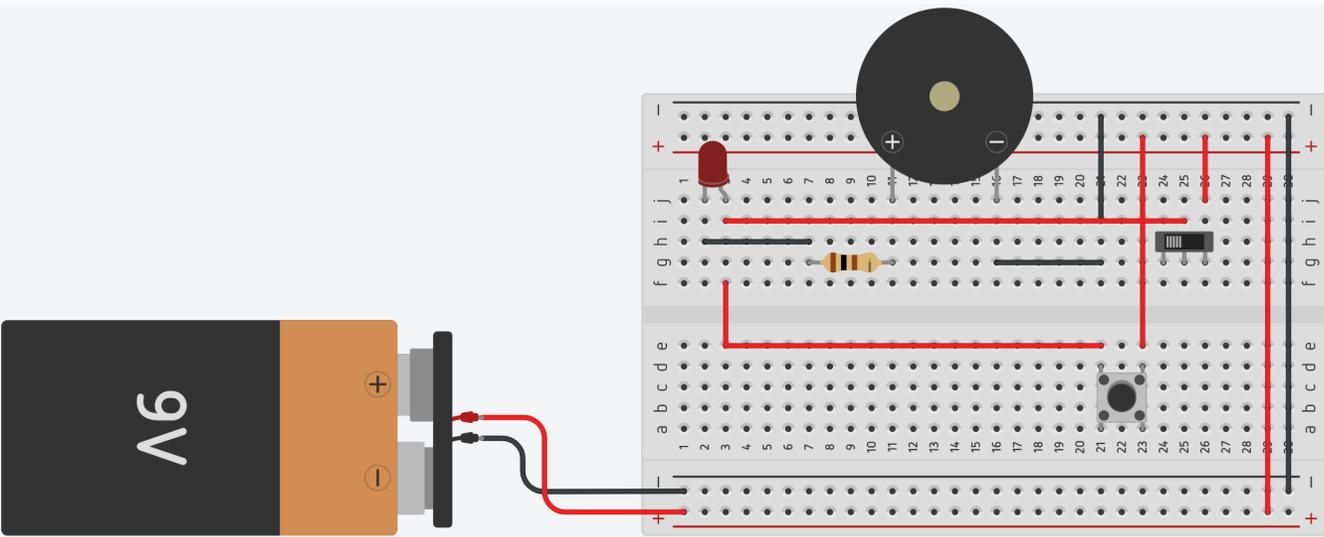


Circuit view

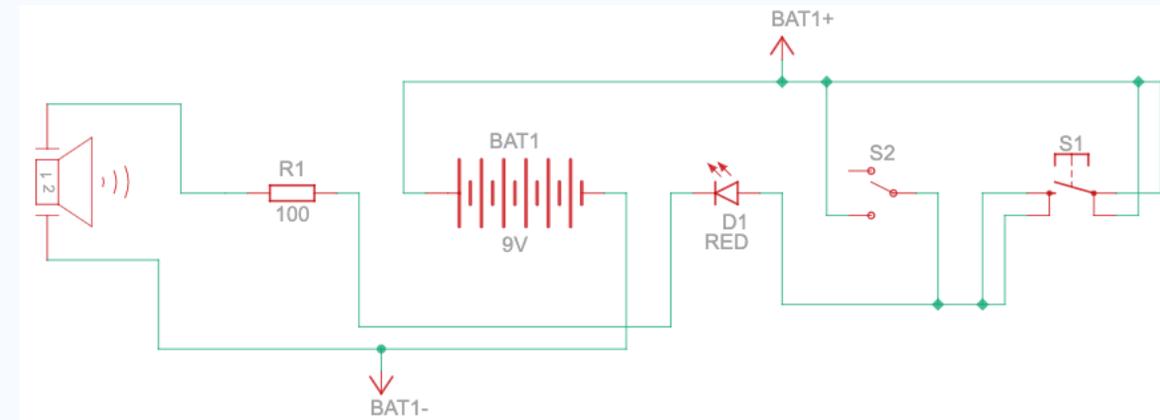


Schematic view

Power source, connectors, breadboard, LED

Circuits – No Toggle, External resistor

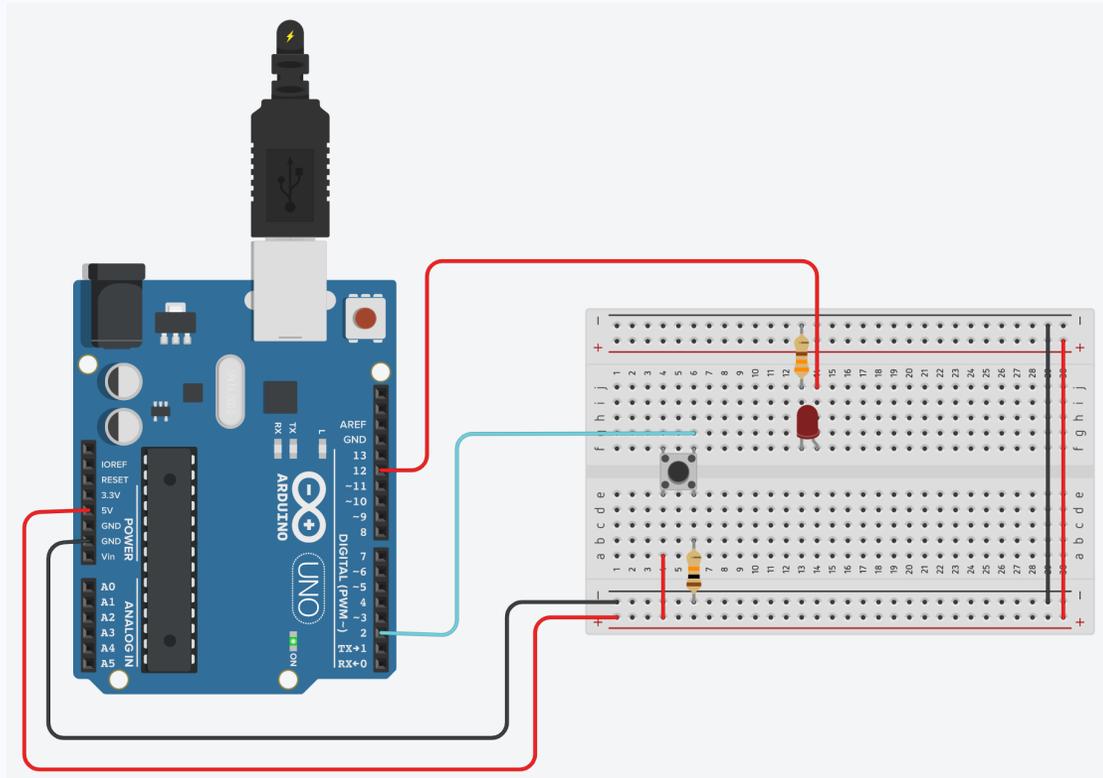

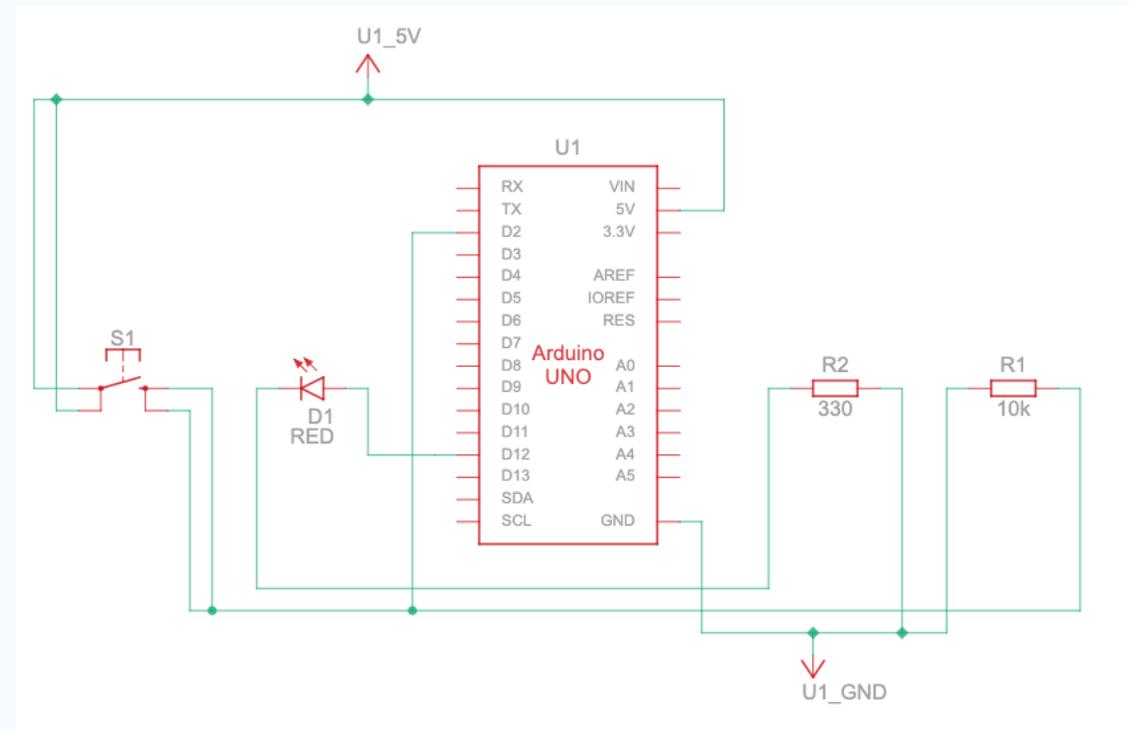
Circuit view – Pull Up Resistor (external)




Schematic view

ON/OFF: controller, pins, connectors, breadboard, resistors (to stop 'bounce'), press switch, LED (N.B. 'HIGH', 'LOW')

Circuits – No Toggle, LED

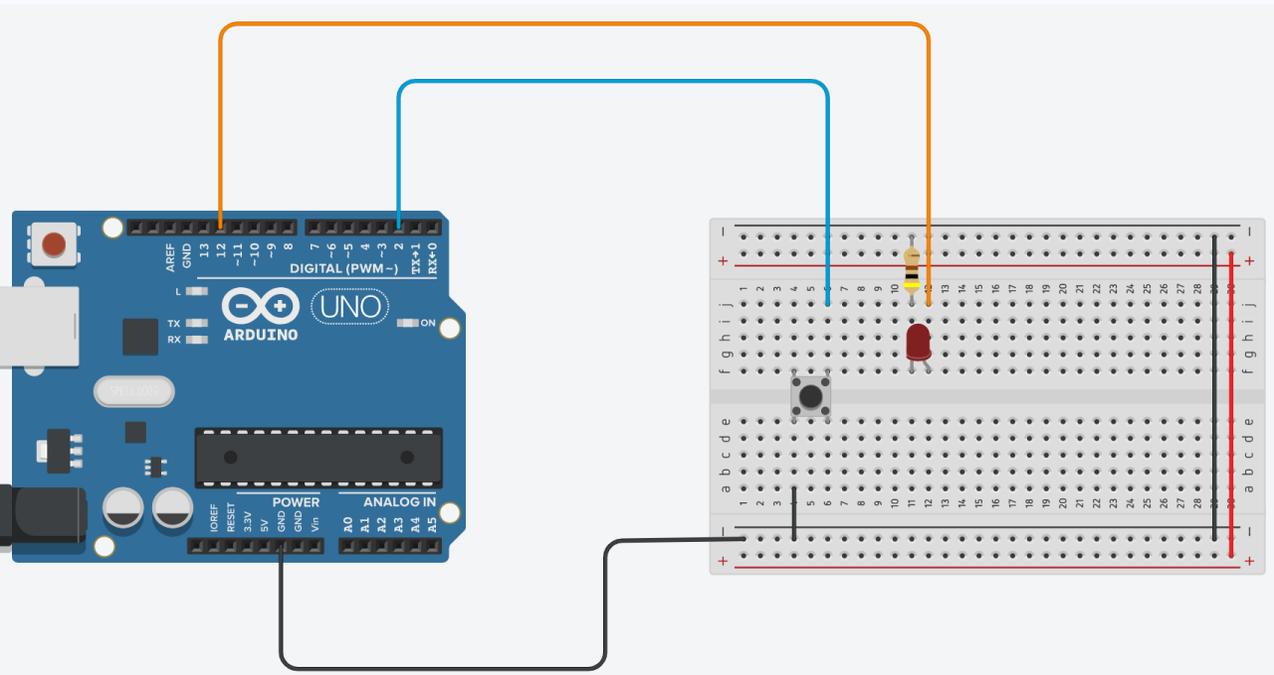


Circuit view – Pull Up Resistor in built

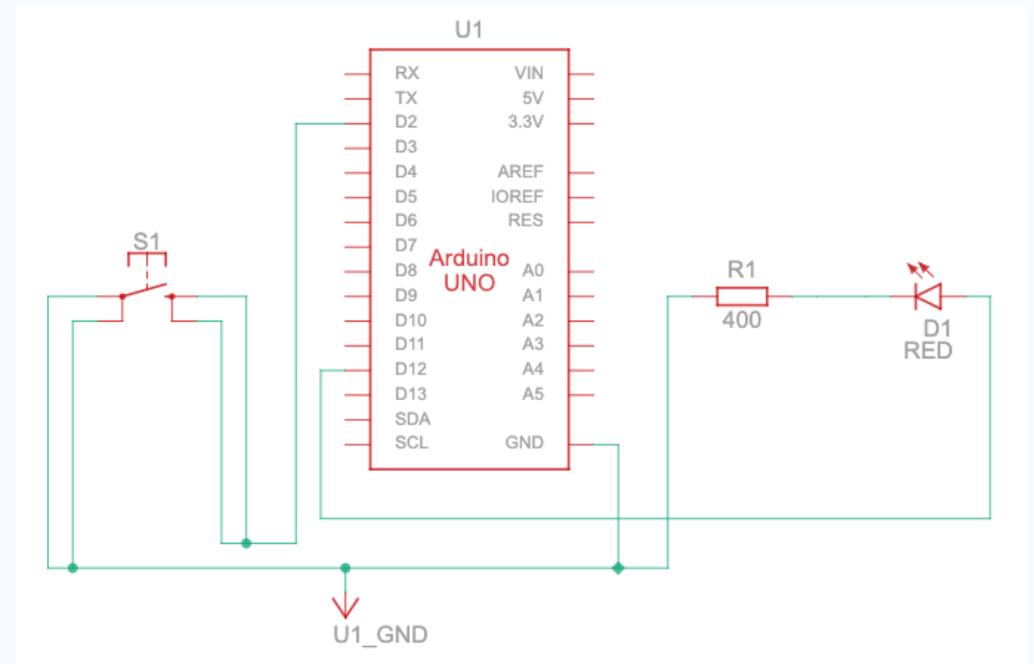


Schematic view

Power source, connectors, breadboard, LED

Circuits – Toggle, LED, State

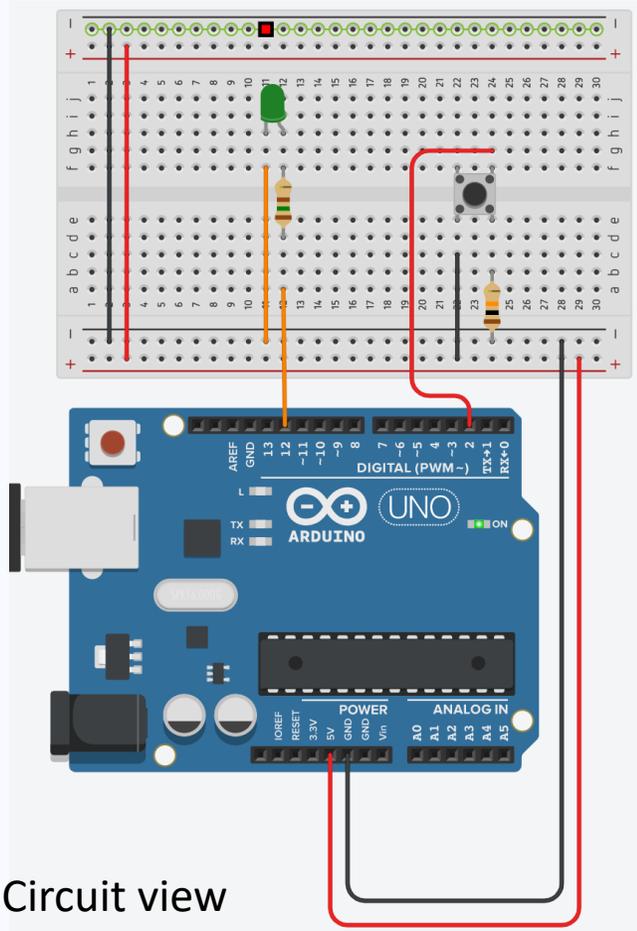


Circuit view

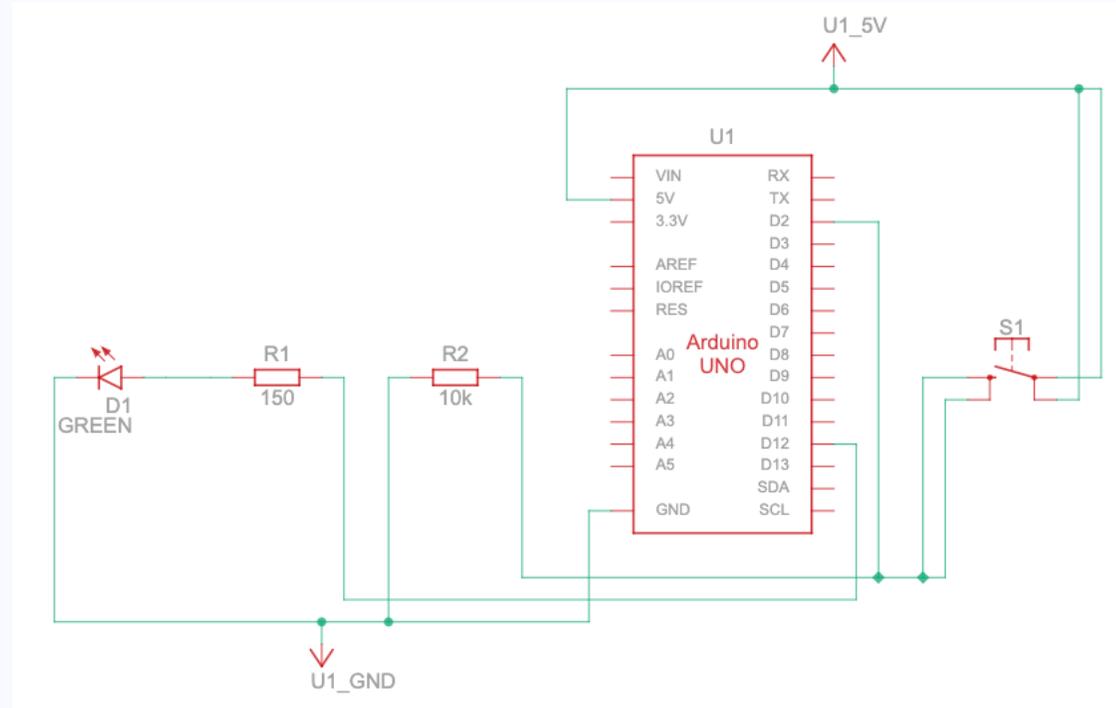


Schematic view

Power source, connectors, breadboard, LED

Circuits – Toggle, LED

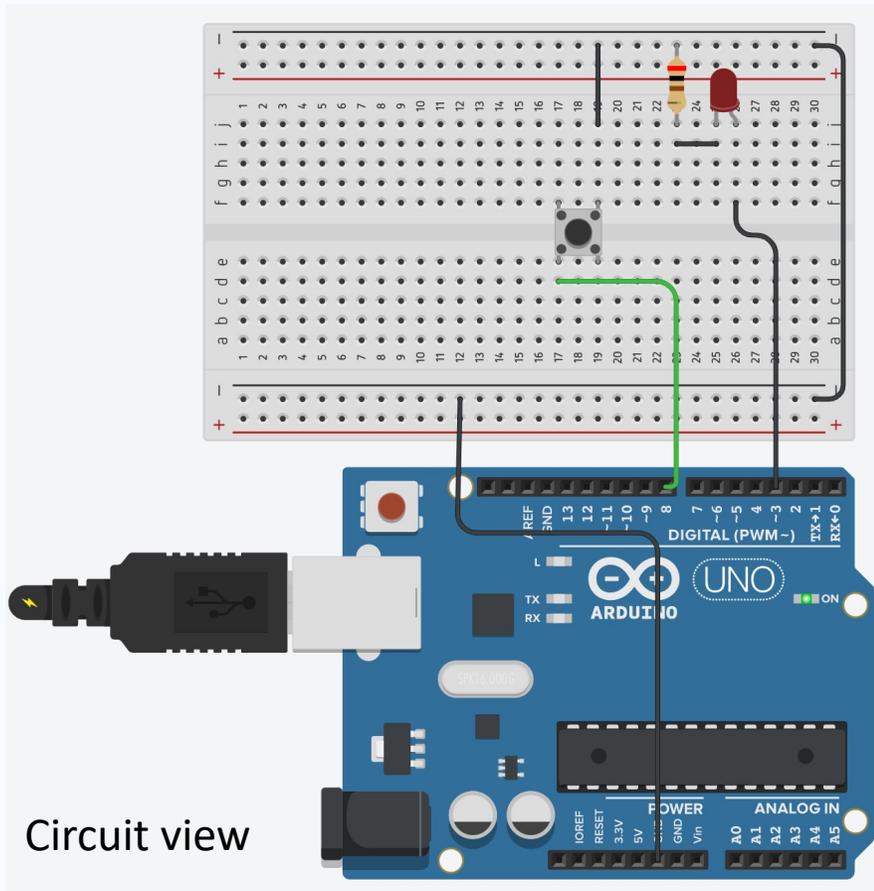


Circuit view

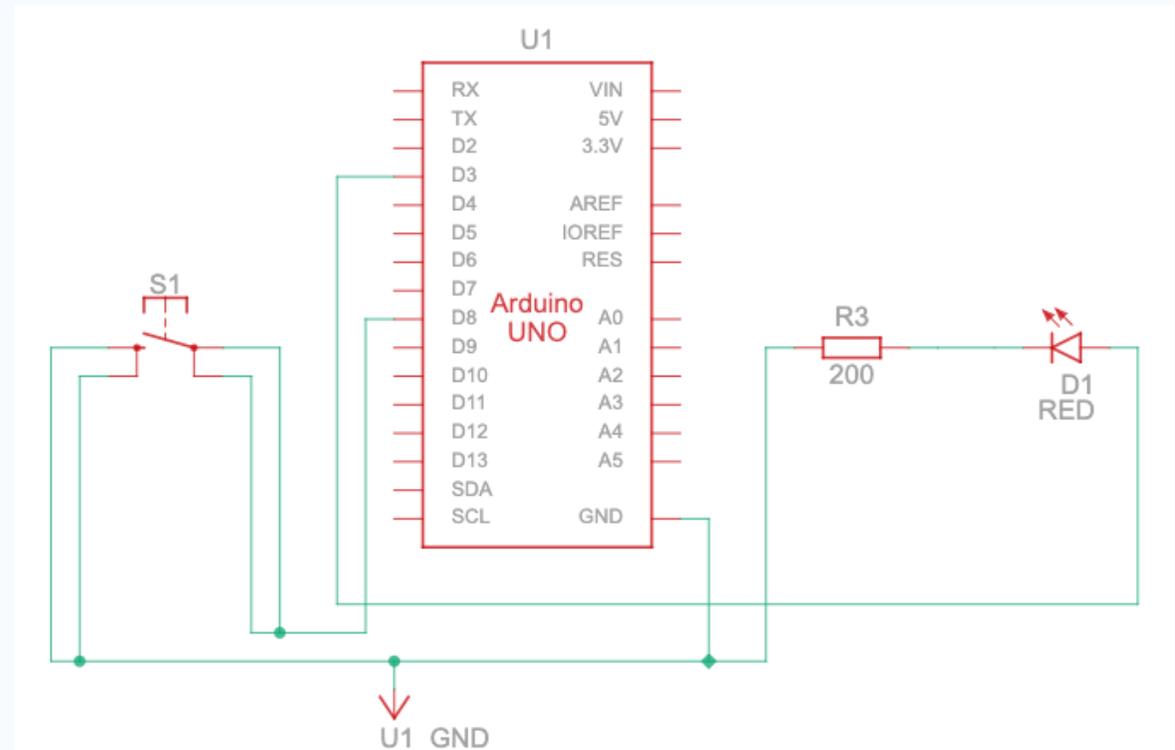


Schematic view

Power source, connectors, breadboard, LED

Circuits – Toggle, LED

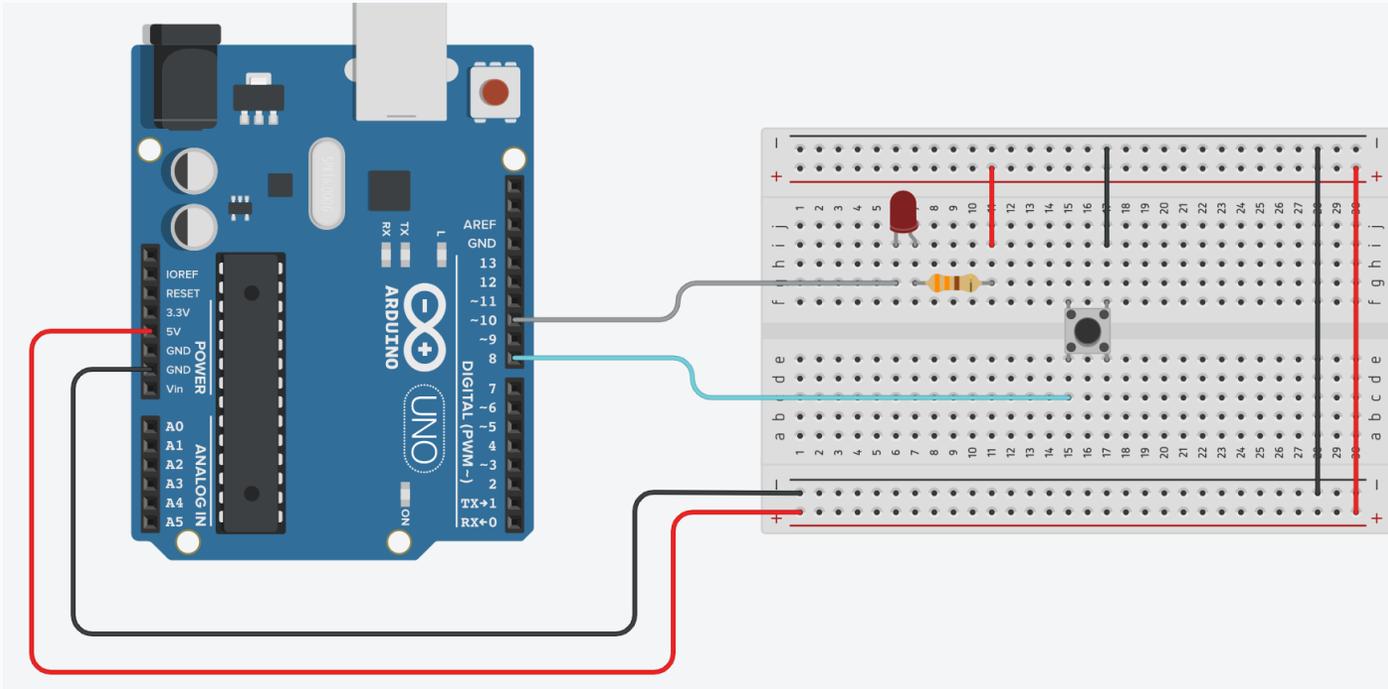


Circuit view

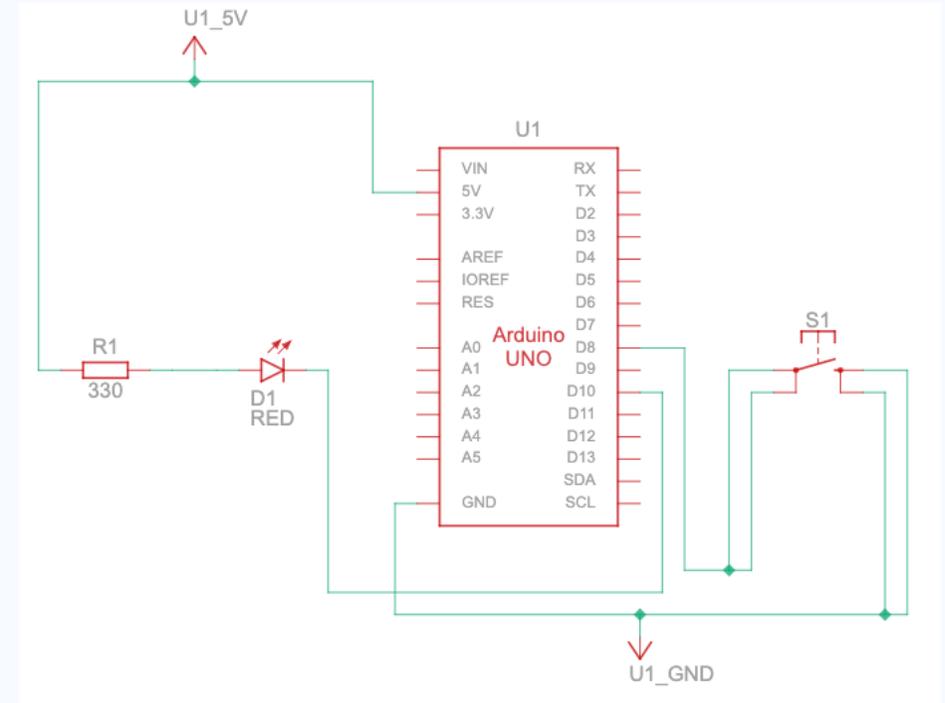

Schematic view


Power source, connectors, breadboard, LED

Circuits – Multiple Components

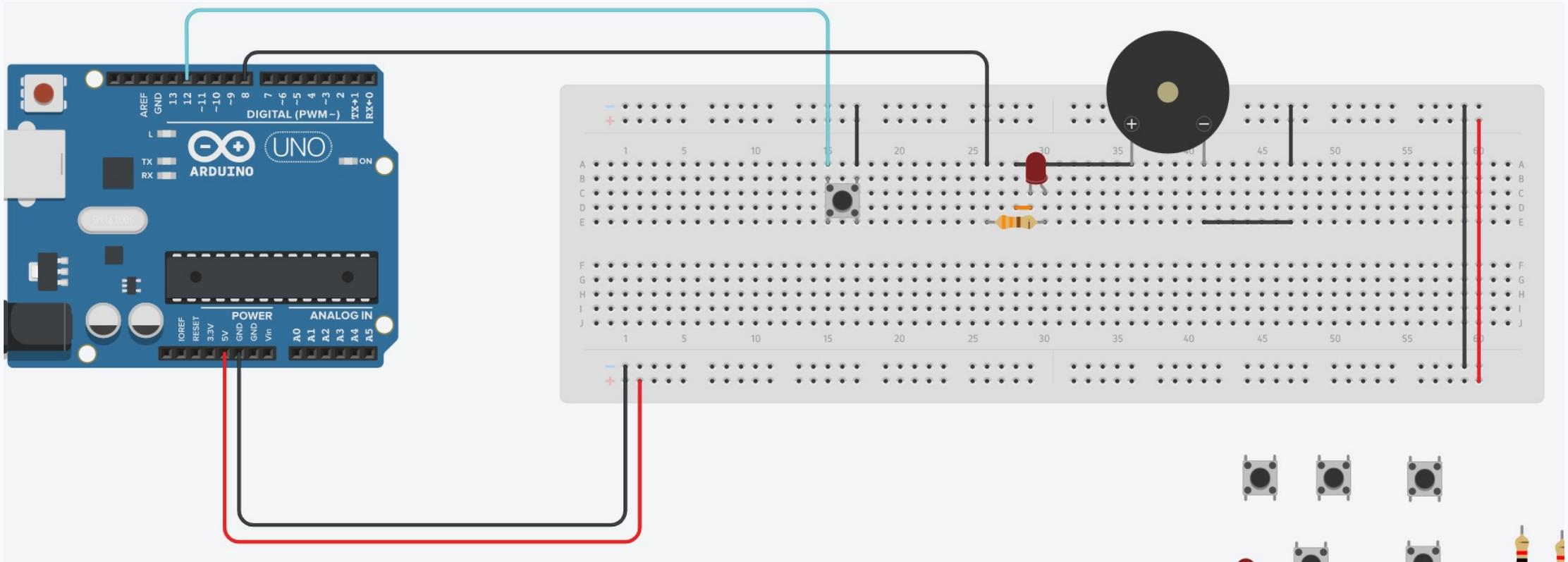

Circuit view
Power source, connectors, breadboard, LED


Circuits – Multiple Components

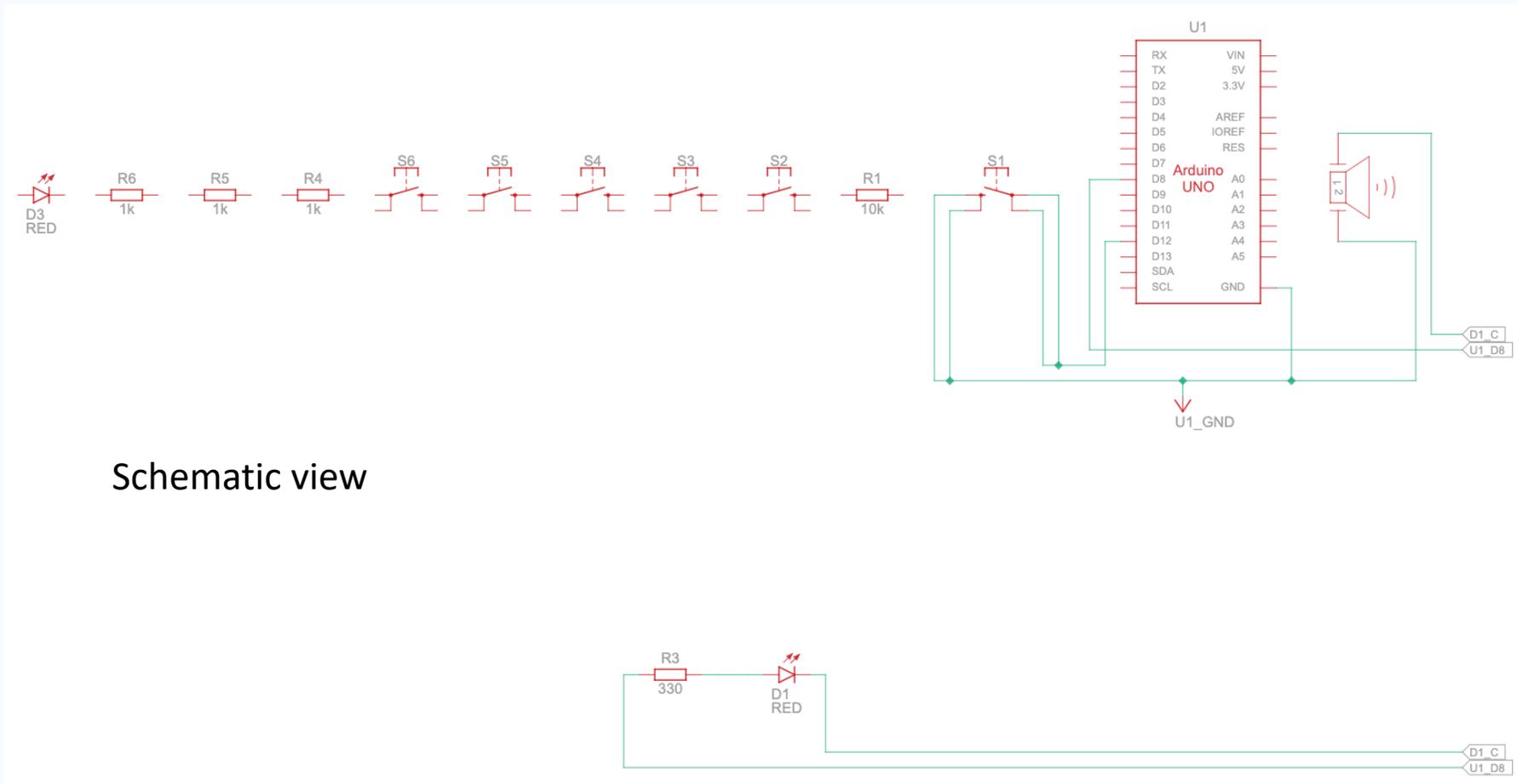

Schematic view


Power source, connectors, breadboard, LED

Circuits – No Toggle, Code Comparison

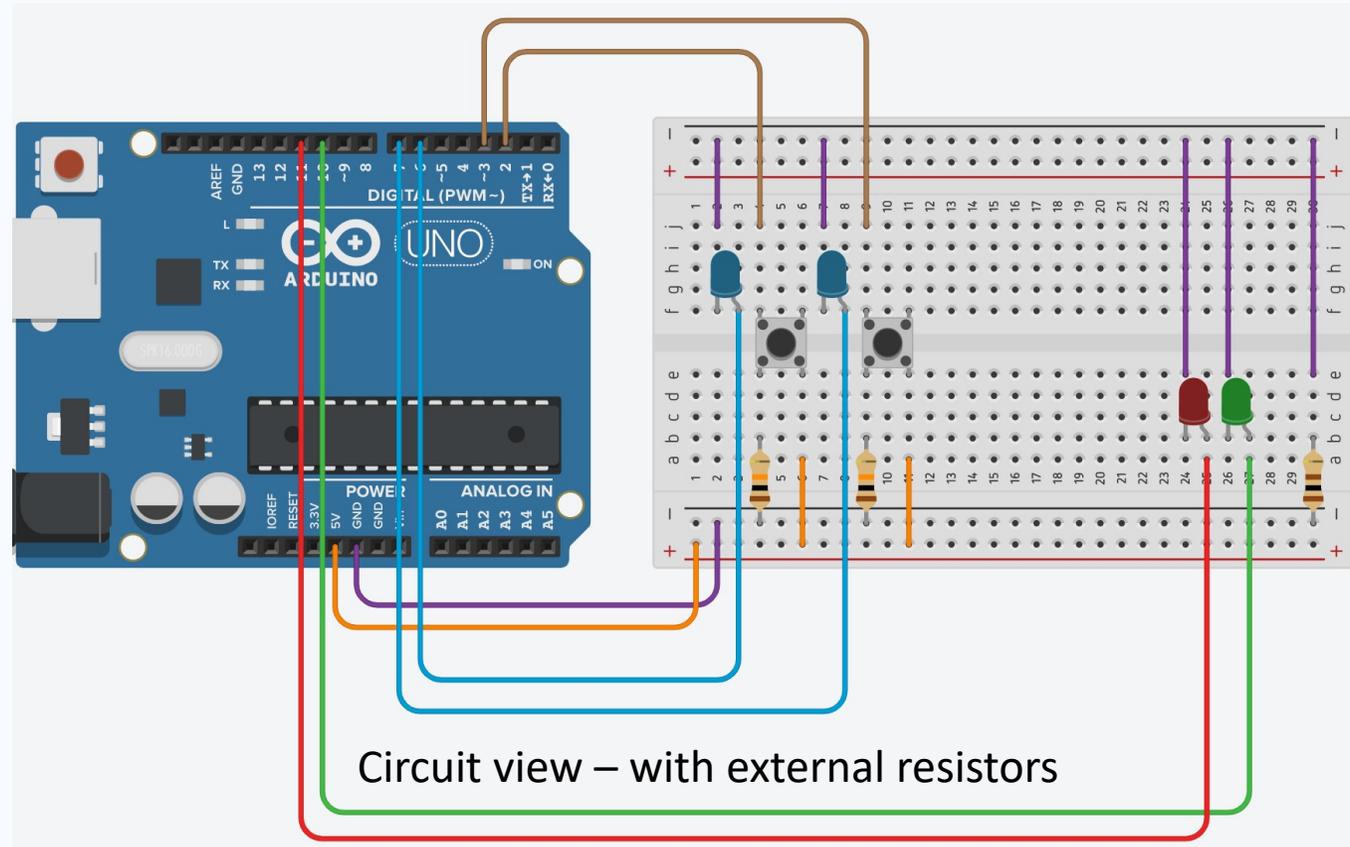


Power source, connectors, breadboard, LED

Circuits – No Toggle, Code Comparison

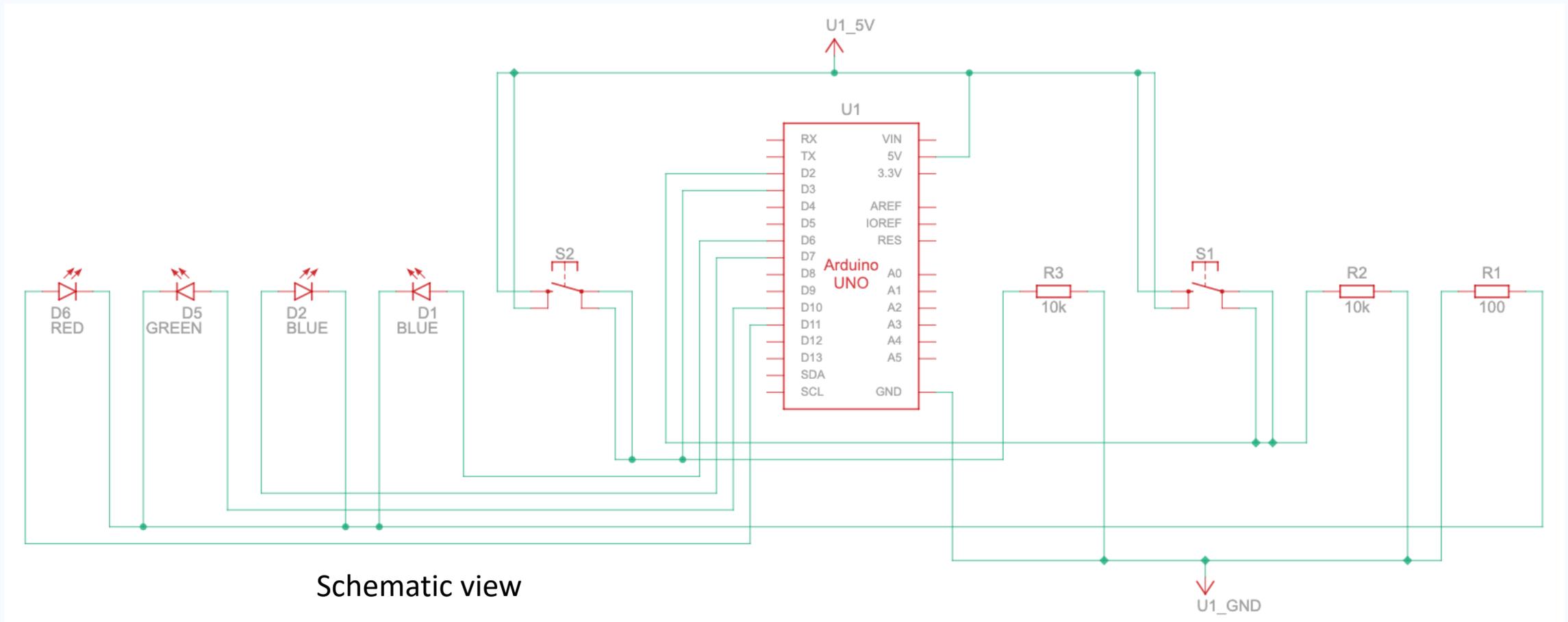


Power source, connectors, breadboard, LED

Circuits – Toggle, ‘jumping’ LEDs

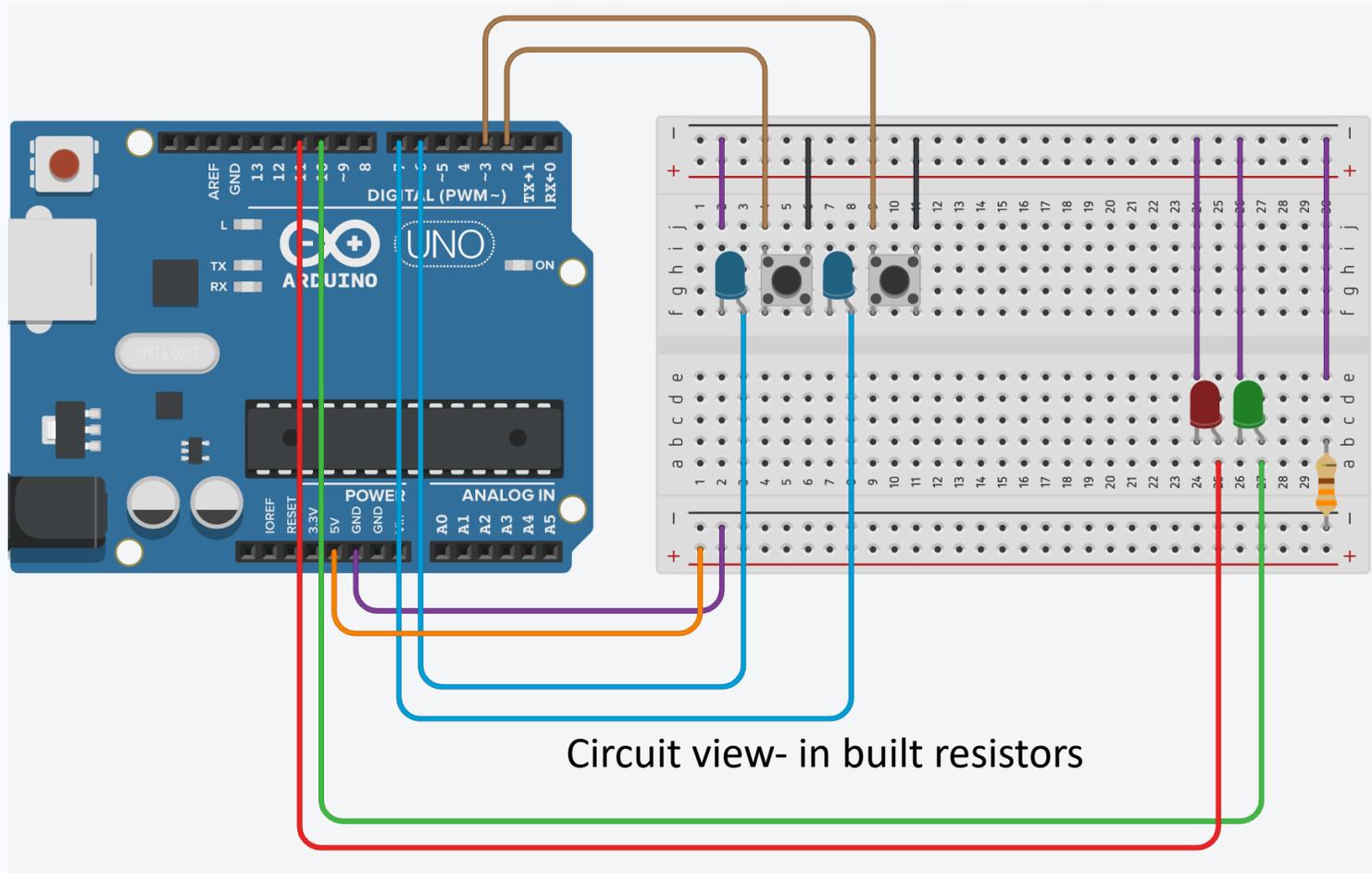


Power source, connectors, breadboard, LED

Circuits – Toggle, ‘jumping’ LEDs

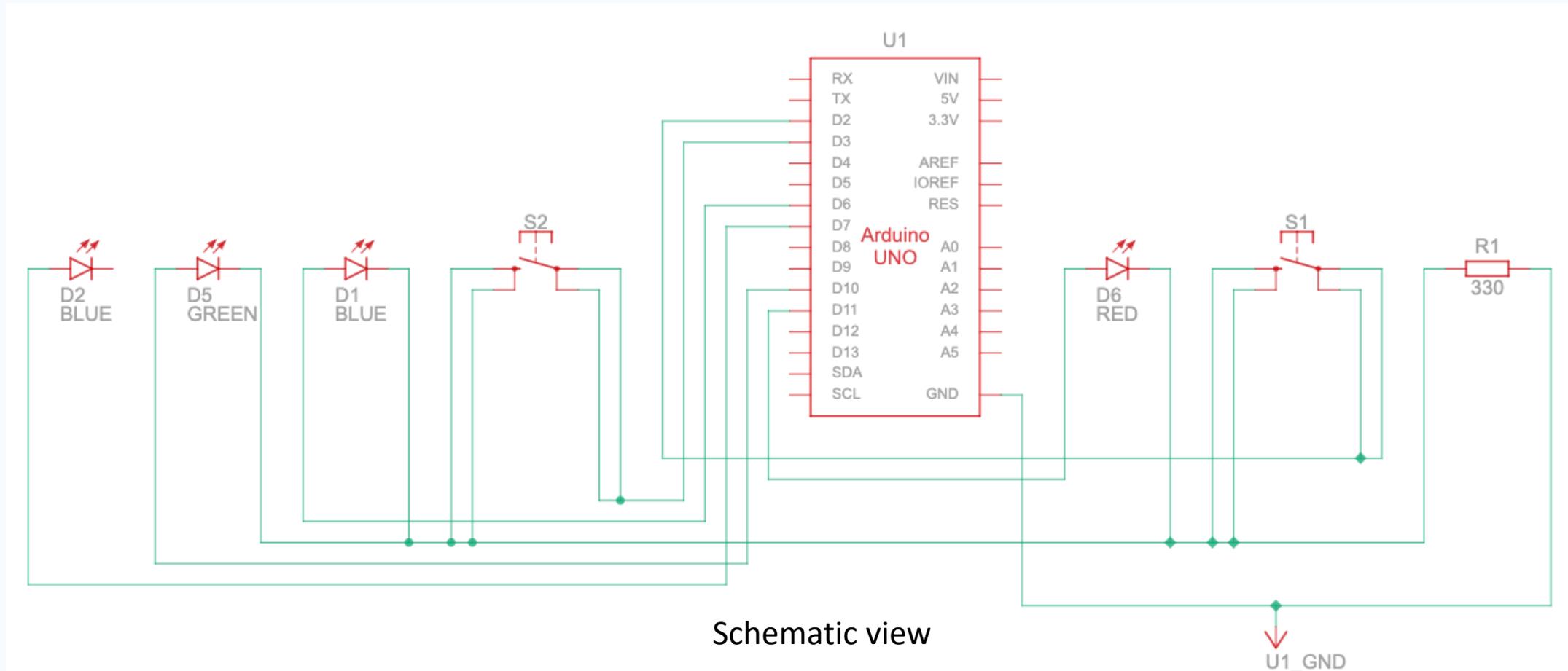

Power source, connectors, breadboard, LED


Circuits – Toggle, LED, expansion

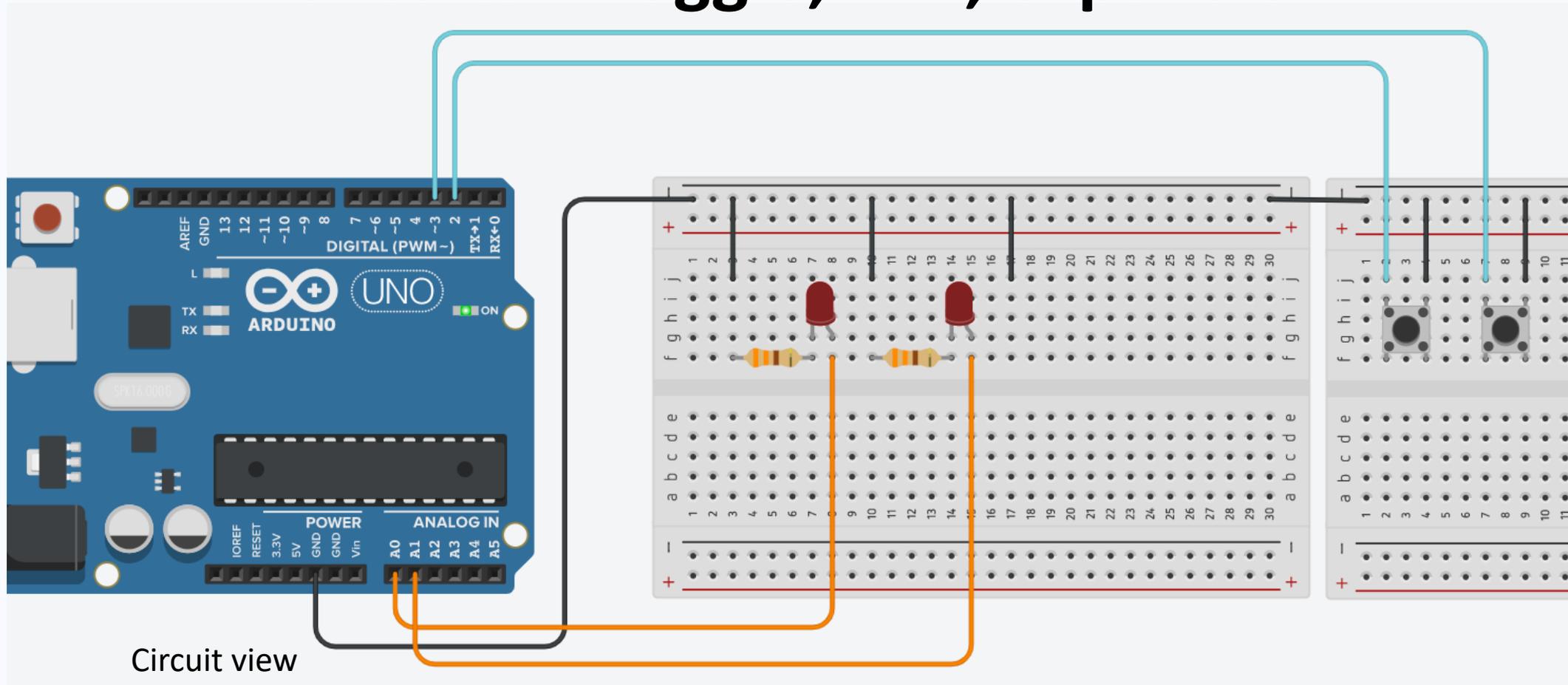

Circuit view


Power source, connectors, breadboard, LED

Circuits – Toggle, LED, expansion

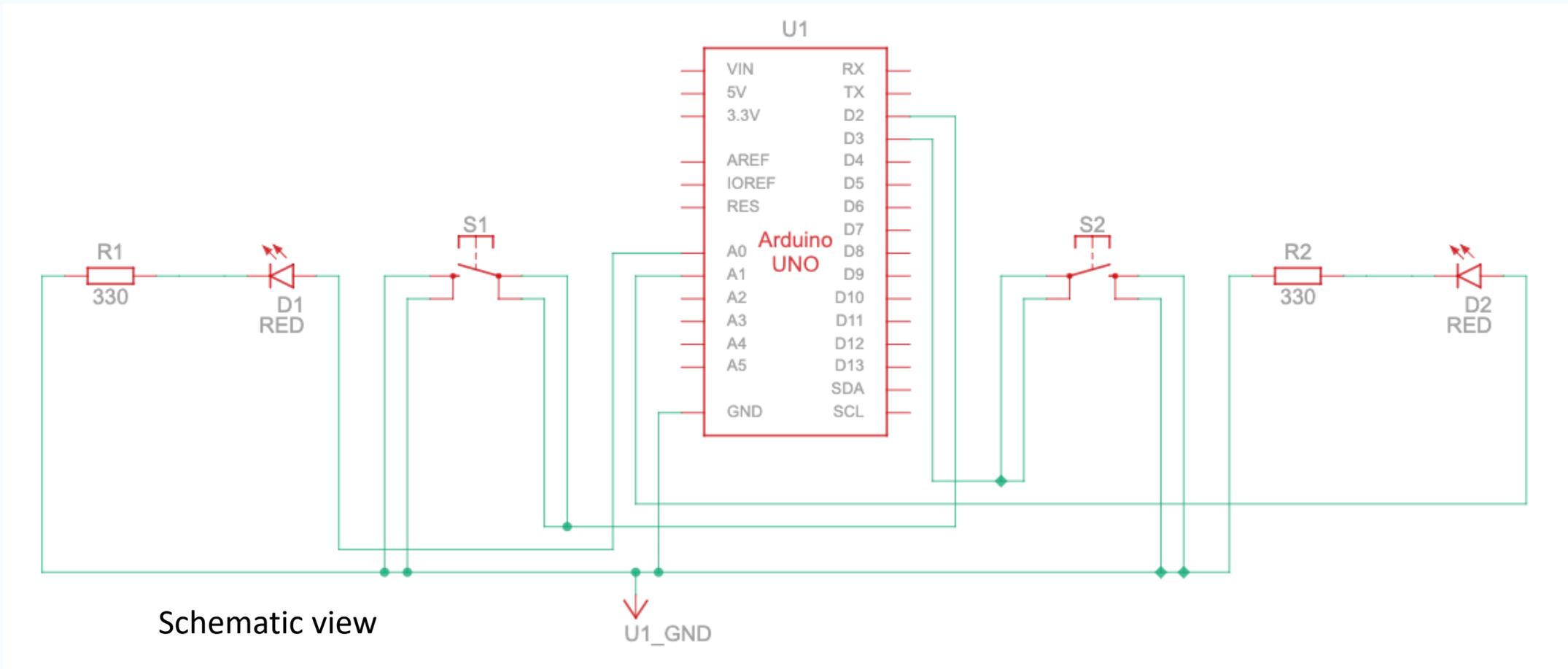


Power source, connectors, breadboard, LED

Circuits – Toggle, LED, expansion

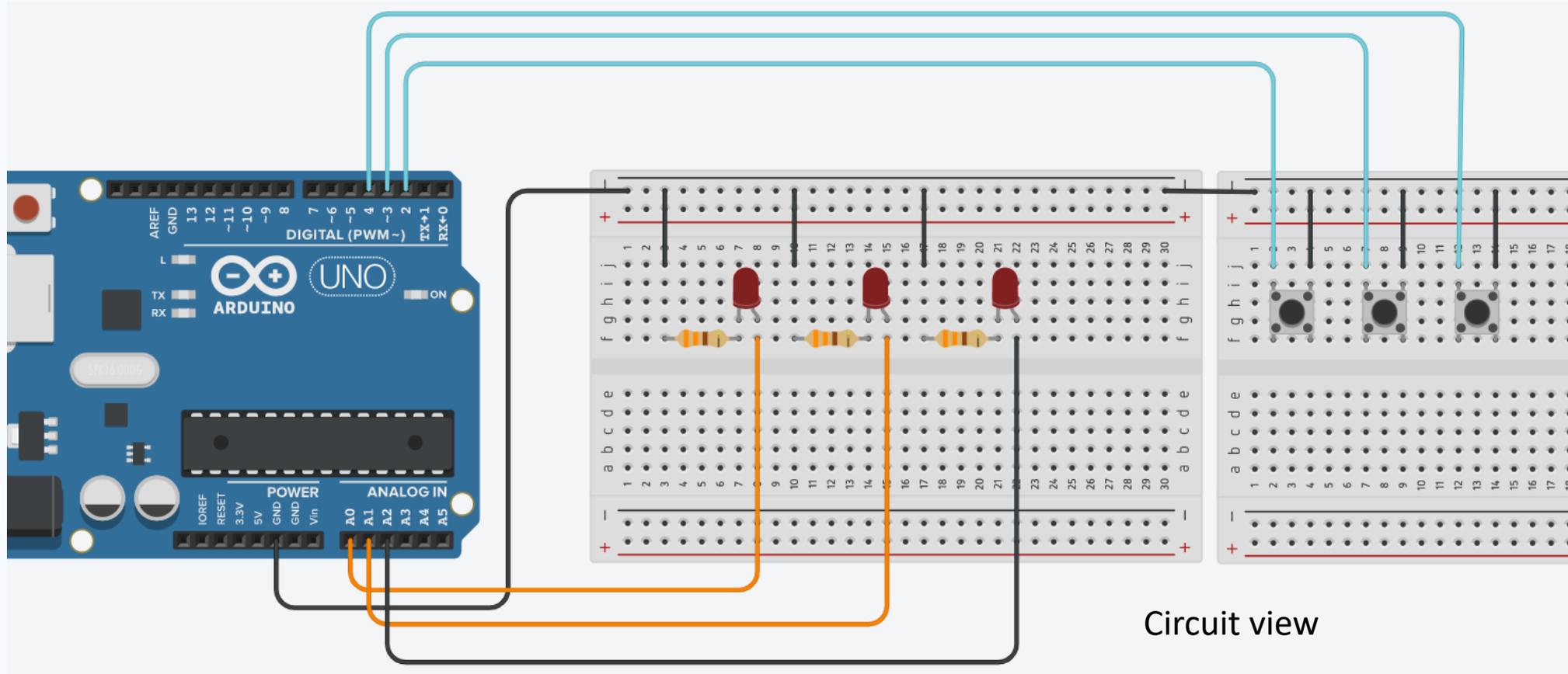


Power source, connectors, breadboard, LED

Circuits – Toggle, LED, expansion

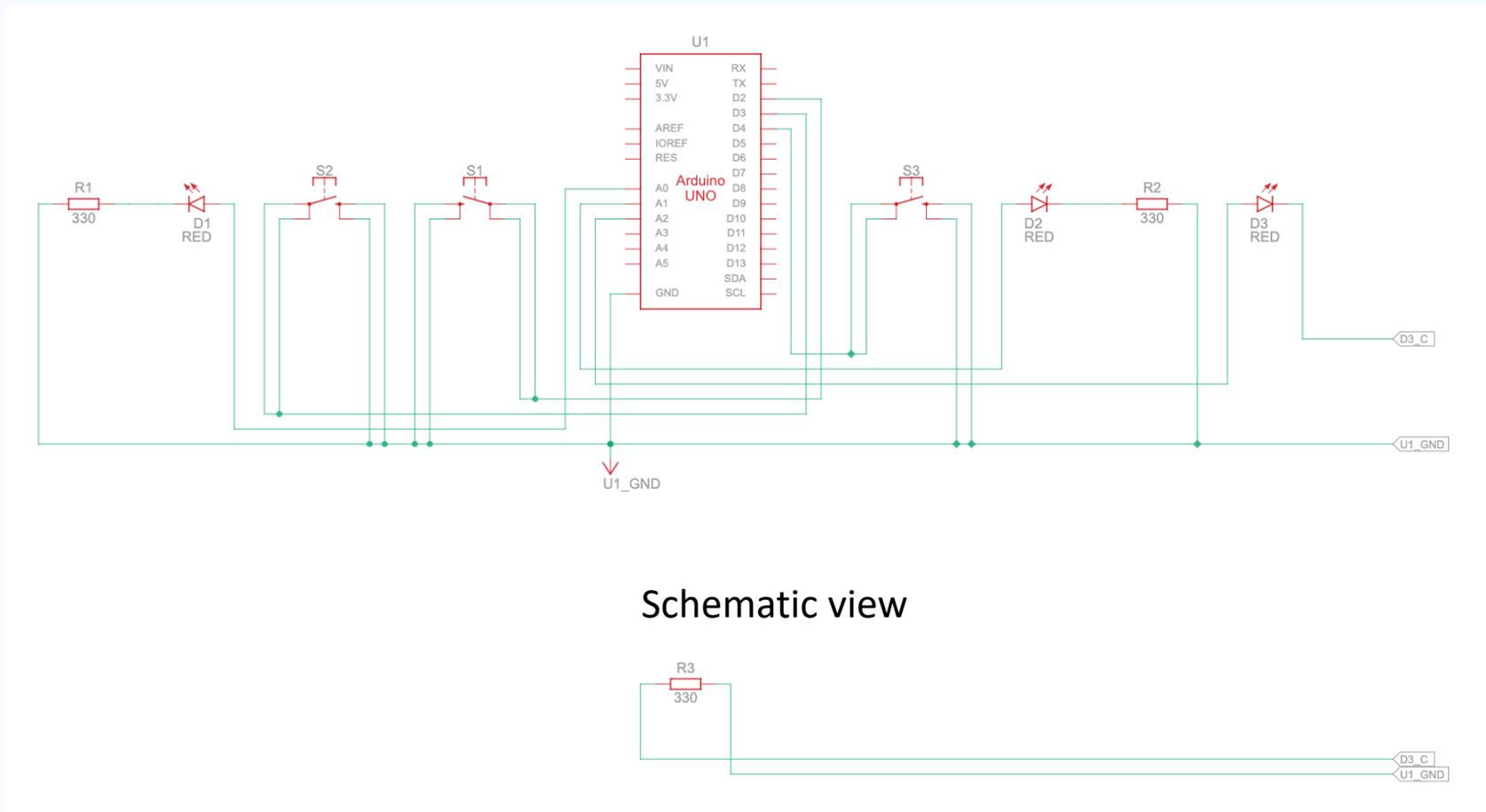


Power source, connectors, breadboard, LED

Circuits – Toggle, LED, Switch

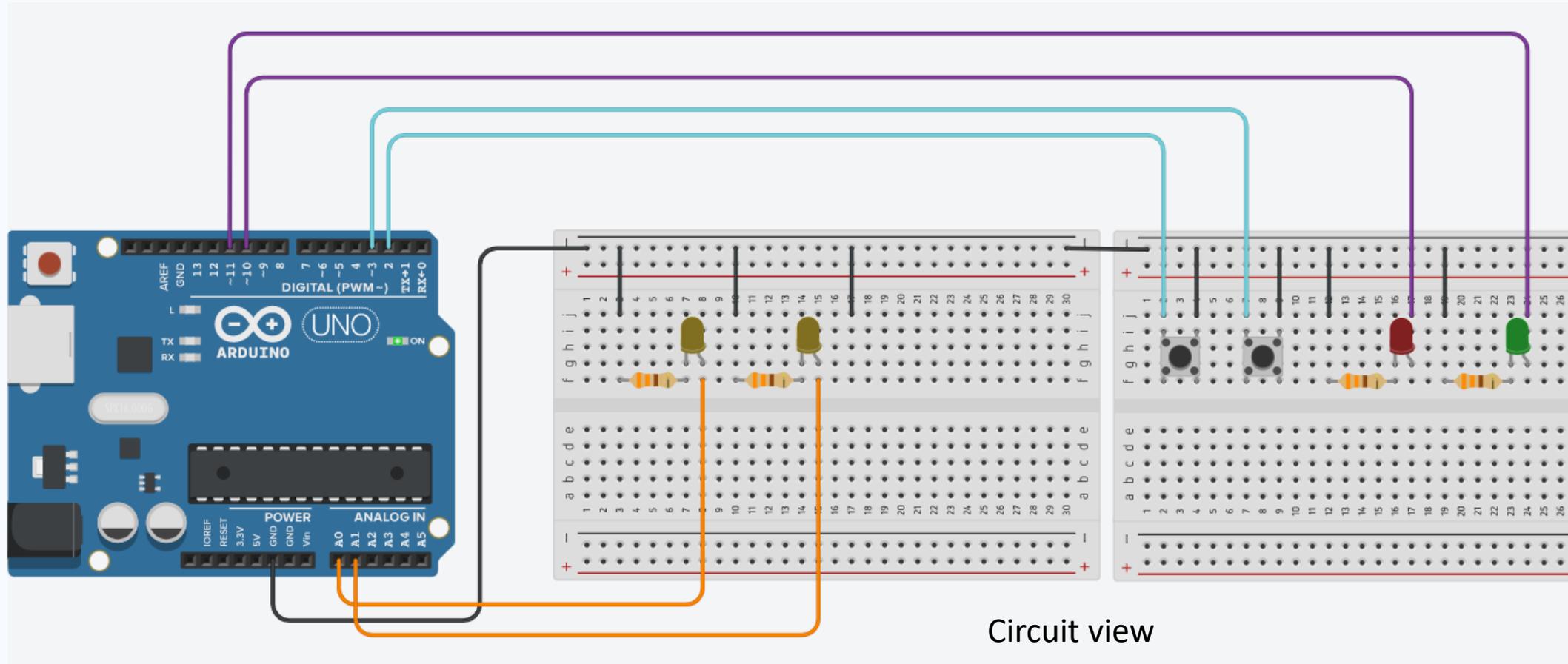


Power source, connectors, breadboard, LED

Circuits – Toggle, LED, Switch

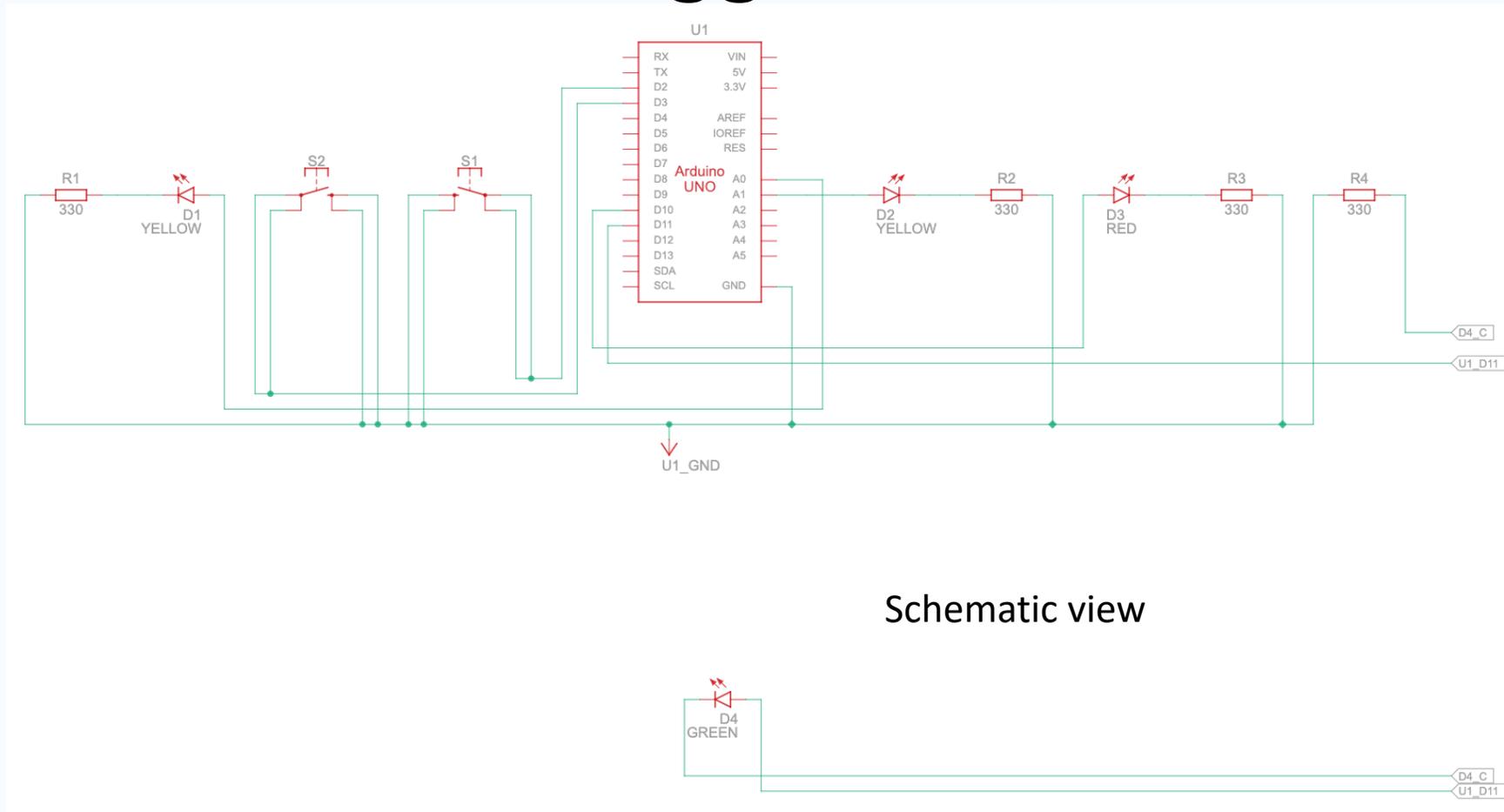


Power source, connectors, breadboard, LED

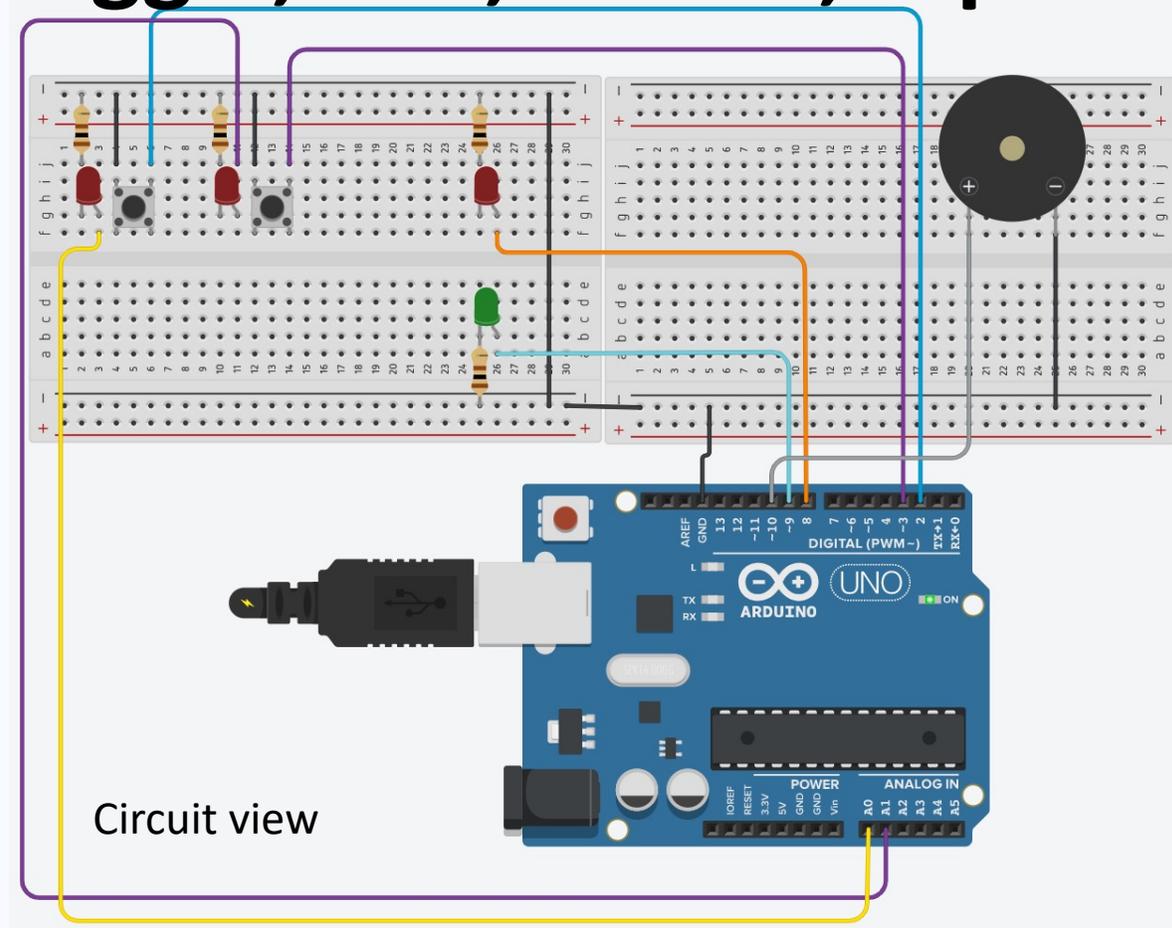Circuits – Toggle, LED, Buzzer, Input Comparison



Power source, connectors, breadboard, LED

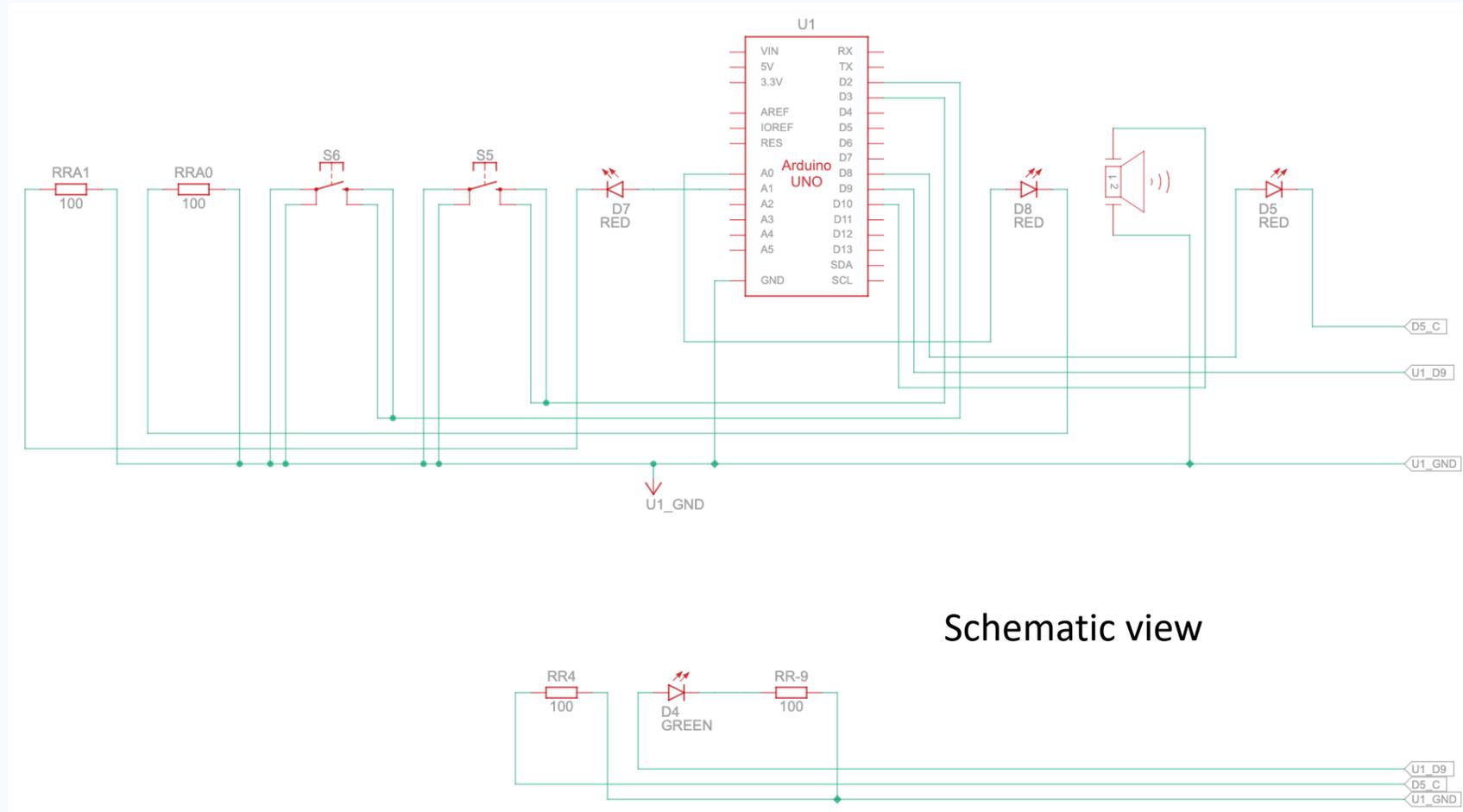Circuits – Toggle, LED, Buzzer, Input Comparison



Power source, connectors, breadboard, LED

Summary

- You can define a basic circuit
- You can explain the concept of a programmable controller
- You can define Pull-Up and Pull-Down resistors and their use
- You can write code to create 'Toggle' switch effect
- You can write code which uses input comparison

CMP-3002A
Foundations of Computing 1

Circuits & Controllers - end

Dr Robert Blair

r.blair@uea.ac.uk
